

國立中央大學100學年度碩士班考試入學試題卷

所別：光電科學與工程學系碩士班 不分組(一般生)

科目：電子學

共 2 頁 第 1 頁

本科考試可使用計算器，廠牌、功能不拘

\*請在試卷答案卷(卡)內作答

1. For the BJT amplifier shown in Figure 1, answer the following questions. The parameters are  $v_b = 5$  V, the current through  $R_2$  is 1 mA,  $|V_A| = 200$  V,  $V_T = 25$  mV, and the base current can be neglected.
  - (a) Find the values of  $R_1$  and  $R_2$ . (6%)
  - (b) Find the bias current of the transistor  $I_C$  ( $V_{BE} = 0.7$  V). (4%)
  - (c) If  $R_3 = 4$  k $\Omega$ , find  $R_{in}$  and  $R_o$ . (10%)
  - (d) Determine the small signal gain  $A_v = v_o/v_s$ . (5%)

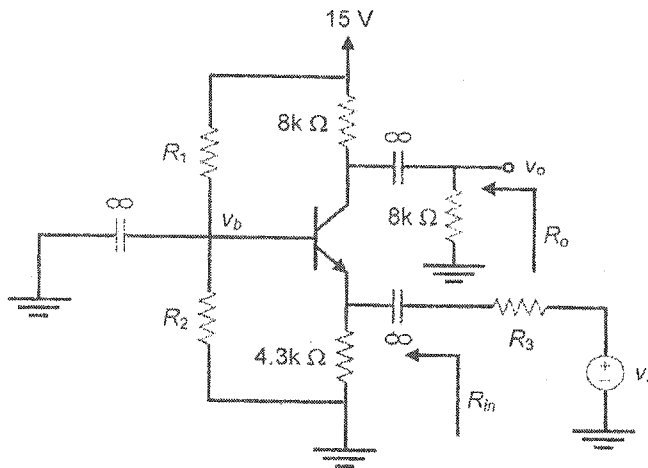


Fig. 1

2. For the active first-order filter shown in Figure 2, answer the following questions:
  - (a) Determine the transfer function  $H(s) = V_o/V_s$ , where  $s = j\omega$ . (5%)
  - (b) What condition is required for the circuit to operate as a highpass filter? (5%)  
Draw the magnitude Bode plot and find the 3-dB frequency. (5%)
  - (c) What condition is required for the circuit to operate as a lowpass filter? (5%)  
Draw the magnitude Bode plot and find the 3-dB frequency. (5%)

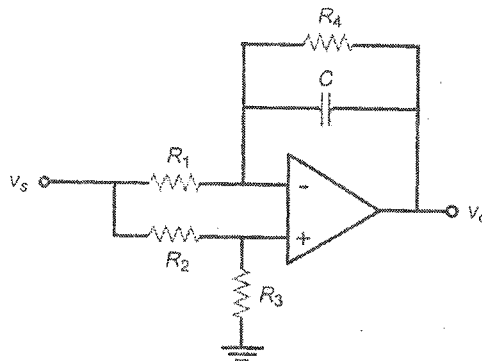


Fig. 2

參考用

注意：背面有試題

參考用

3. Consider the circuit shown in Figure 3. The forward-bias cut-in voltage of the diode is  $V_{TH}$  and the forward-bias resistance is  $r_f$ .
- (5%) (a) Determine the minimal electric current in LED.
  - (5%) (b) Determine the maximal electric current in LED.

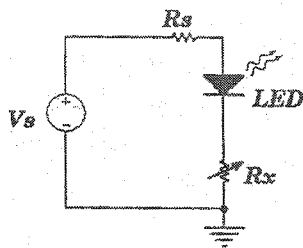


Fig. 3:

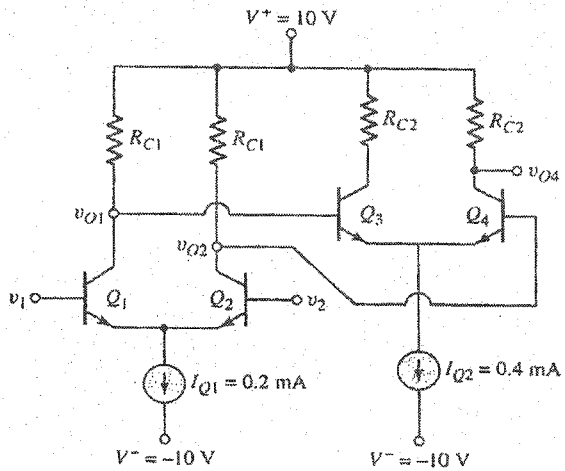


Fig. 4:

4. Consider the circuit shown in Fig. 4. The parameters are  $\beta = 180$  and  $V_A = \infty$ .  $v_{O1} = v_{O2} = 2$  V and  $v_{O4} = 6$  V when  $v_1 = v_2 = 0$  V.
- (5%) (a) Determine the value of  $R_{C1}$ .
  - (5%) (b) Determine the value of  $R_{C2}$ .
  - (5%) (c) Determine the differential-mode voltage gain  $A_{d1} = (v_{O1} - v_{O2}) / (v_1 - v_2)$ .
  - (5%) (d) Determine the differential-mode voltage gain  $A_d = v_{O4} / (v_1 - v_2)$ .
5. Consider the phase-shift oscillator in Figure 5.
- (5%) (a) Derive the expression for the frequency of oscillation.
  - (5%) (b) Determine the condition for oscillation.
  - (5%) (c) For  $R = 20$  k $\Omega$ , find  $C$  and  $R_F$  that will produce sustained oscillations at  $f_o = 22$  kHz.
  - (5%) (d) Sketch the Bode phase plot.

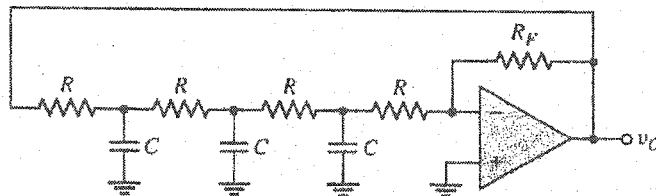


Fig. 5

注意：背面有試題