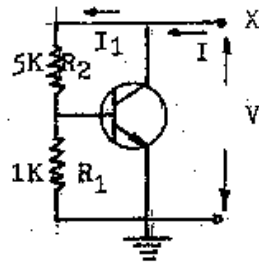


國立中央大學八十九學年度碩士班研究生入學試題卷

所別： 光電科學研究所 不分组 科目： 電子學 共 1 頁 第 1 頁

1. The V_{BE} multiplier. Find the values of V and the incremental resistance between x and ground? (20%)



$$V_{BE} = 0.7V$$


$$I = 10 \text{ mA}$$

$$h_{fe} = 500$$

$$h_{ie} = 10K$$

$$h_{re} = h_{oe} = 0.$$

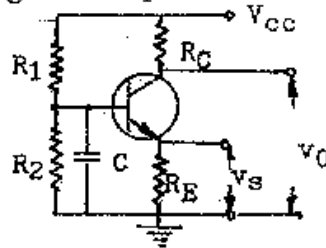
2. The amplifier as shown. Find voltage gain, input and output impedance. (20%)



Assume: $h_{re} = h_{oe} = 0$

參考用

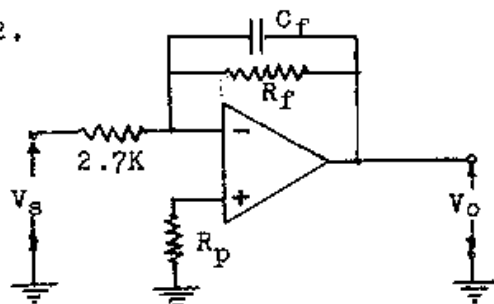3. Design the OP-amp. RC circuit to realize a low-pass filter with a corner frequency of 20 KHz. and low-frequency gain of 12. (20%)



4. An OP-amp has a rated output voltage of $\pm 12 \text{ V}$ and a slew rate of $1 \text{ V}/\mu\text{s}$. What is its full-power bandwidth? If an input sinusoid with frequency $f = 5f_M$ is applied to a unity-gain follower constructed this OP-amp. What is the maximum possible amplitude that can be accommodated at the output without incurring slew-induced distortion? (20%)
- ($f_M =$ full-power bandwidth.)

5. The difference amplifier as shown. Find voltage gain. (20%)

