

國立中央大學99學年度碩士班考試入學試題卷

所別：光電科學與工程學系碩士班 不分組(一般生)

科目：電子學 共 2 頁 第 1 頁

本科考試禁用計算器

*請在試卷答案卷(卡)內作答

- For the circuit in Figure 1, the parameters are $V_{TN} = 1.5\text{V}$ and $K_n = 0.5\text{ mA/V}^2$ for transistors M_1 and M_2 .
 - Determine that I_D , V_{GS1} , V_{DS1} , V_{GS2} , and V_{DS2} for transistors M_1 and M_2 , respectively.
 - Sketch the load line for transistor M_2 .
 - Sketch the current-voltage characteristics of transistor M_1 .

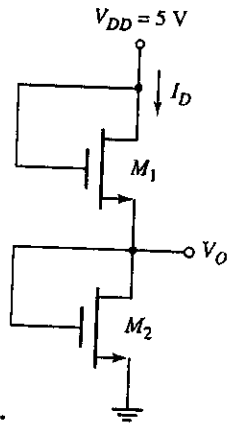


Fig. 1:

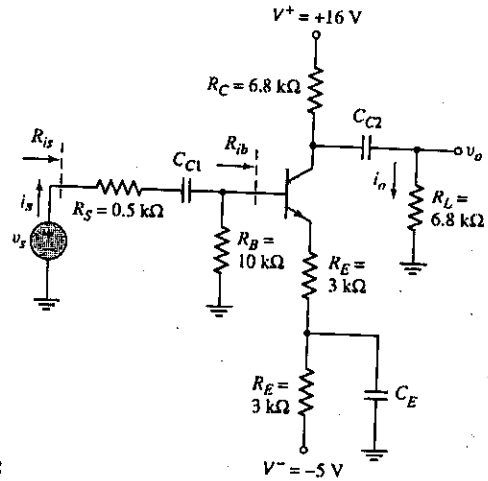


Fig. 2:

- Consider the circuit shown in Fig. 2. The parameters are $\beta = 150$ and $V_A = \infty$.
 - Determine the small-signal voltage gain $A_v = v_o/v_s$.
 - Determine the small-signal current gain $A_i = i_o/i_s$.
 - Find the input resistance R_{ib} .
 - Find the input resistance R_{is} .
- A multistage amplifier is shown in Figure 3. The transistor parameters for M_1 are $V_{TN} = 0.5\text{ V}$, $K_n = 2\text{ mA/V}^2$, and $\lambda = 0$, and for M_2 , M_3 , and M_4 are $V_{TP} = -0.5\text{ V}$, $K_p = 1\text{ mA/V}^2$, and $\lambda = 0$. Let $V_{DD} = 10\text{ V}$, $V^+ = 10\text{ V}$, and $V^- = -10\text{ V}$, $I_{Bias} = 0.1\text{ mA}$. The resistor parameters are $R_S = 10\text{ k}\Omega$, $R_D = 5\text{ k}\Omega$, $R_G = 500\text{ k}\Omega$, and $R_L = 5\text{ k}\Omega$. The capacitor parameters are $C_{gs} = 10\text{ pF}$, $C_{gd} = 2\text{ pF}$ for all transistors, C_G and C_S approaching infinite in the small signal circuit, and $C_C = 5\text{ }\mu\text{F}$ for all coupling capacitors.
 - Determine the lower 3 dB frequency.
 - Determine the upper 3 dB frequency.
 - Determine the midband voltage gain.

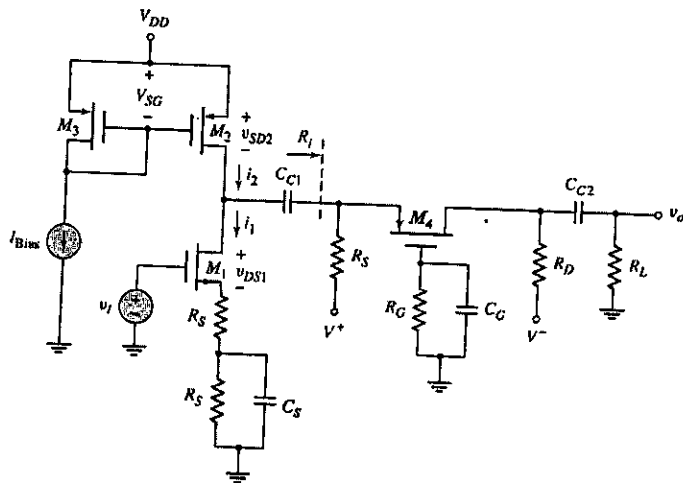


Fig. 3:

注意：背面有試題

參考用

4. A signal generating circuit is shown in Figure 4. The high saturated output voltage of the comparator is V_H and the low one is V_L .
- (2%) (a) Find the relation between the voltage V_x and the output voltage V_o .
 - (3%) (b) Find the relation between the voltage V_c and the output voltage V_o .
 - (5%) (c) Draw the time diagram for the voltages V_c and V_o , respectively.
 - (5%) (d) Determine the frequency and the duty cycle of the output voltage V_o .

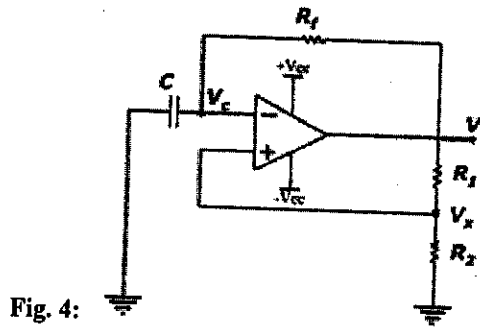


Fig. 4:

5. The figure 5 shows the circuit for a constant current driver. The normal driving condition for LED is set at 700mA. For Q_1 , $\beta=100$, $V_{BE}=0.75V$, $V_{CE,sat}=0.2V$ and $V_{CE,breakdown}=50V$.
- (5%) (a) Why can it be a constant current driver? Derive the relation between the driving voltage V_1 and the output current to drive LED.
 - (5%) (b) What are the proper values for the resistor R_1 and the reference voltage V_1 ?
 - (5%) (c) As under 700mA driving, the forward voltage of the LED is 3.0V. What is the **maximal number** of the LEDs in series such that the constant current driver can still normally operate?

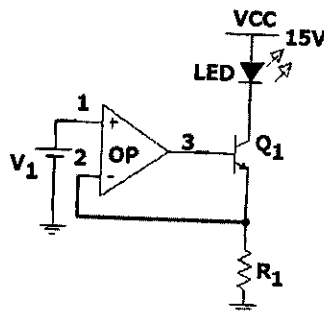


Fig. 5:

6. A second-order filter circuit is shown in Figure 6.
- (10%) (a) Derive the transfer function, V_o/V_i .
 - (5%) (b) What are the requirements for the circuit being a low-pass filter?
 - (5%) (c) What are the requirements for the circuit being a high-pass filter?

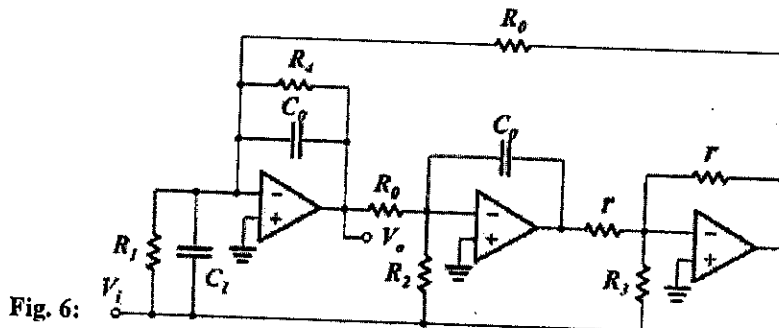


Fig. 6:

參考用

注意：背面有試題