

九十四學年度電機系碩士在職專班試題卷

共 2 頁 第 1 頁

科目：基礎電子學

應考時間：100 分鐘

選擇題 (每題 5 分)

1. 對一理想的電壓放大器而言，下列何者敘述有誤？(A) 輸入阻抗愈大愈佳 (B) 輸出阻抗愈大愈佳 (C) 電壓增益愈大愈佳 (D) 以上皆非。
2. 下列何者敘述有誤？(A) 共射極(common-emitter)放大器之電壓增益遠小於 1 (B) 共集極(common-collector or emitter follower)放大器有極大的輸出阻抗 (C) 共基極放大器(common-base)之電流增益遠大於 1 (D) 以上皆非。
3. 對一 pn 二極體而言，下列何者敘述為真？(A) 順向電流隨溫度增加而增加 (B) 逆向電流隨溫度增加而減小 (C) 順向偏壓之介面電容(junction capacitance)小於逆向偏壓之介面電容 (D) 以上皆真。
4. 對一互補式金氧半電晶體反相器(CMOS inverter)而言，下列何者敘述有誤？(A) 由 n-MOSFET 與 p-MOSFET 共同組成 (B) 功率損耗較 nMOS inverter 大 (C) noise margin 較 nMOS inverter 大 (D) 以上皆非。
5. 對一金氧半電晶體(MOSFET)而言，下列何者敘述為真？(A) 為一四端點(four terminals)元件(B) enhancement-mode nMOSFET 之臨限電壓(threshold voltage, V_{th})大於 0 V (C) 在相同的元件結構與幾何大小下，nMOSFET 之電流高於 pMOSFET (D) 以上皆真。
6. 若將二個 pn 二極體串接如 Fig. 1，在何種偏壓條件下可表現出雙載子電晶體(BJT)的特性？(A) $V_{BE} > 0$ 且 $V_{BC} < 0$ (B) $V_{BE} < 0$ 且 $V_{BC} < 0$ (C) $V_{BE} > 0$ 且 $V_{BC} > 0$ (D) 以上皆非。

 


Fig. 1 Circuit for Problem 6.

 


Fig. 2 Circuit for Problem 7.

 


Fig. 3 Circuit for Problem 8

7. (16 分) Use the superposition principle to find the output voltage of the circuit shown in Fig. 2.
8. (16 分) Consider a BJT current mirror, as shown in Fig. 3, with a nominal current transfer ratio of unity. Let the transistors have $V_{BE} = 0.7$ V, $I_S = 10^{-15}$ A, $\beta = 100$, and $V_A = 100$ V. For $I_{REF} = 1$ mA, find I_O when $V_O = 5$ V. Also, find the output resistance.
9. (26 分)
For a dc voltage of 1 V applied to the input of the shown basic switched-capacitor integrator (Fig. 4) in which the ϕ_1 and ϕ_2 are 1 MHz two-phase nonoverlapping clock.
 - (a) (4 分) What charge is transferred for each clock cycle?
 - (b) (4 分) What is the average current drawn from the input source?
 - (c) (4 分) What is the equivalent resistance seen by the input source?
 - (d) (4 分) What change in output for each clock cycle? In what direction?
 - (e) (5 分) For an amplifier saturating at ± 10 V, how many cycles does it take for the amplifier output to go from one limit to the other?
 - (f) (5 分) What is the average slope of the output?

九十四學年度電機系碩士在職專班試題卷 共 2 頁 第 2 頁

科目：基礎電子學

應考時間：100 分鐘

10. (12 分) In usual applications of the shown logic circuit in Fig. 5, the signal C acts as a clock, being normally held high while X, Y and Z change. Finally, C falls while X, Y and Z are stable.
- (a) (6 分) For signals having 0 V and 5 V levels and using positive logic convention, express F as a function of C, X, Y, Z.
- (b) (6 分) For dynamic operation of the shown circuit equivalent to that of a basic symmetric inverter with $(W/L)_n = 4 \mu\text{m}/2 \mu\text{m}$ and $(W/L)_p = 8 \mu\text{m}/2 \mu\text{m}$, choose appropriate device widths, assuming that all device lengths are $2 \mu\text{m}$.

 


Fig. 4 Circuit for Problem 9.

 


Fig. 5 Circuit for Problem 10.