

類組：電機類 科目：數位邏輯(300H)

共10頁第1頁

※請在答案卷內作答

考生請注意：

- 本試卷共有 20 題試題。每題 5 分。
- 你的答案必須如下圖所示由上而下依序寫在答案卷的作答區。
- 只要填寫考題所要求的答案，請勿附加計算過程。

從此處開始寫起

1. (a), (b).

2. (c), (d).

3. 15

4. (1) 1, (2) 0

5. $Z = B + AC'$

、 、 、

參考用

注意：背面有試題

類組：電機類 科目：數位邏輯(300H)共 10 頁 第 2 頁

※請在答案卷內作答

Question 1 [5pt]. Convert 63.2_7 to a number with base 16.

Question 2 [5pt]. Which of the following equations are valid? (Multiple choices)

- (a) $A'B'C+B'CD'+EF'=(B'+E)(B'+F')(C+E)(C+F')(A'+D'+E)(A'+D'+F')$
- (b) $WXY'+(W\equiv X)+(Y\oplus W)=(X+Y)\oplus W$
- (c) $[(A'+B)'+(A'B'C)'+C'D]'=A'B'C$
- (d) $H'I'+JK=(H'+I')(K'+J)(H'+K)(I'+K)$

Question 3 [5pt]. Which of the following statements is always true? (Multiple choices)

- (a) If $AD'+BD'=CD'$, then $AE+BE=CE$.
- (b) If $A\equiv B$ is always true, then $A(X'+Y+Z')=B(X'+Y+Z')$ is always valid.
- (c) If $A\oplus B$ is always true, and $AX=BY$ is always valid, then XY must be false.
- (d) If $A+C=B+C$, then $AZ=BZ$.

Question 4 [5pt]. A combinational circuit has three binary inputs (A,B,C) and two binary outputs (X,Y). XY_2 represents a binary number whose value equals the number of 1's at the input. For example, if $ABC=011$, then $XY=10$. Choose the correct minterms to form the m-notation of X, where the order of literals for m-notation is ABC. (Multiple choices)

- (a) m_0 (b) m_1 (c) m_2 (d) m_3 (e) m_4 (f) m_5 (g) m_6 (h) m_7

※請在答案卷內作答

Question 5 [5pt]. The Karnaugh map below shows the function F with four inputs (A, B, C, D), where A is the most significant bit and D is the least significant bit.

		AB			
		00	01	11	10
CD	00	X	1	X	0
	01	0	X	0	X
	11	X	1	X	1
	10	0	X	1	X

參考用

Which of the following statements is true? (Multiple choices)

- (a) If minterm $m_{13} = 1$, then $F = 0$.
- (b) If $F = 0$, then maxterms $M_4 = M_7 = M_{11} = M_{14} = 1$.
- (c) If minterms $m_1 = m_2 = m_8 = m_{13} = 0$, then $F = 1$.
- (d) $A'C'D'$, $BC'D'$, $A'B$, CD , BC , AC are prime implicants of F .
- (e) F has more than six prime implicants.
- (f) F has no essential prime implicant.


Question 6 [5pt]. Given $F(A, B, C, D) = \prod M(0, 1, 2, 8, 14) \cdot \prod D(3, 5, 7, 9, 10, 15)$. Which of the following statements is true? (Multiple choices)

- (a) The minimum sum of product (SoP) for F is unique.
- (b) The minimum sum of product (SoP) for F is $A'B + BC' + CD$.
- (c) The minimum product of sum (PoS) for F is $(B + D) \cdot (A' + C' + D) \cdot (A + B)$.
- (d) The minimum sum of product (SoP) for F is $A'B + BC' + AD$.
- (e) The minimum product of sum (PoS) for F is $(B + D) \cdot (A' + C' + D) \cdot (B + C)$.
- (f) Boolean expressions respectively shown in (b) and (c) are equivalent.
- (g) Boolean expressions respectively shown in (b) and (e) are equivalent.
- (h) F has more than three minimum product of sum (PoS) solutions.

注意：背面有試題

※請在答案卷內作答

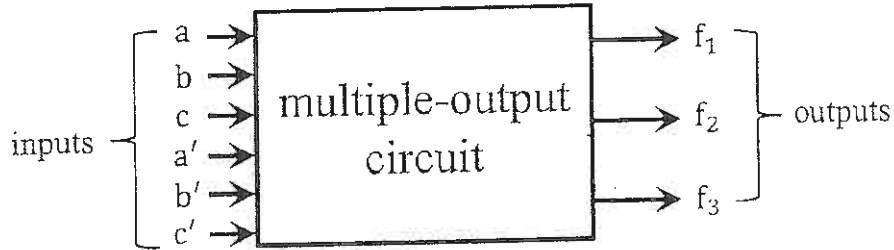Question 7 [5pt]. Choose the circuits which can realize the multiple-output circuit shown in the following figure. (Multiple choices)







The Karnaugh map for each output function is given below.

		f_1	
		$a=0$	$a=1$
bc	00	1	1
	01	1	0
bc	11	0	0
	10	1	0

		f_2	
		$a=0$	$a=1$
bc	00	1	0
	01	1	0
bc	11	0	1
	10	1	0

		f_3	
		$a=0$	$a=1$
bc	00	1	1
	01	0	0
bc	11	0	1
	10	0	0


參考用

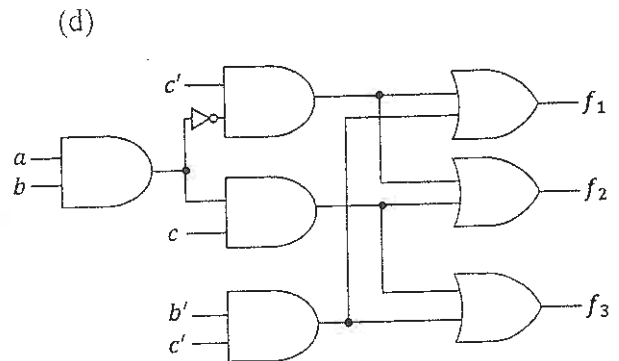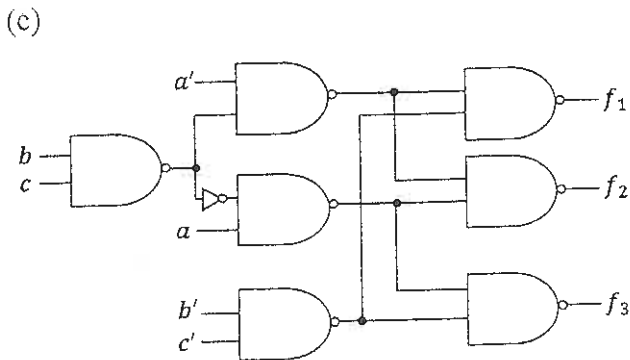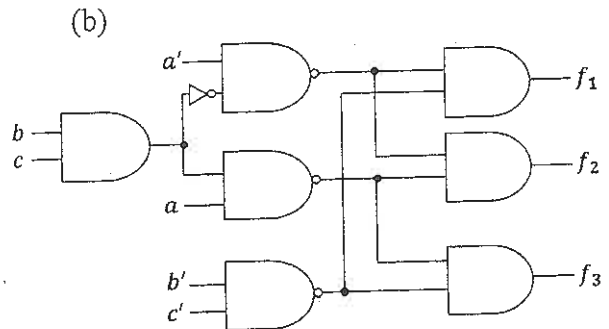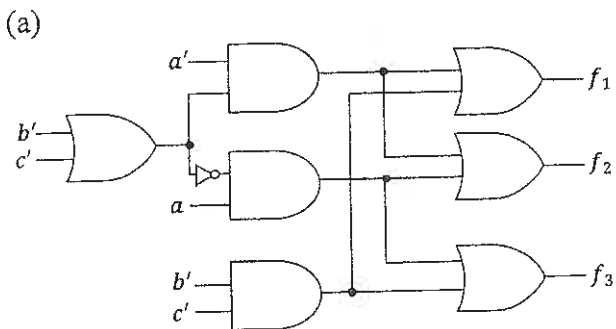

注意：背面有試題

※請在答案卷內作答

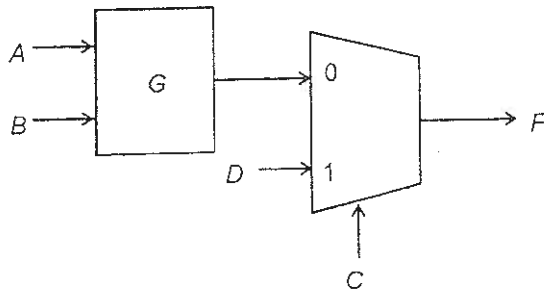
Question 8 [5pt]. Suppose a Boolean function F is implemented by the following circuit with a multiplexor and some unknown function G . In addition, F is partially known shown in the following Karnaugh map. What is the possible function of F in terms of minimum sum of products?



		AB			
		00	01	11	10
CD	00	?	?	1	?
	01	1	?	?	0
	11	?	?	?	?
	10	?	?	?	?

Question 9 [5pt]. What is the corresponding function of G in Question 8?

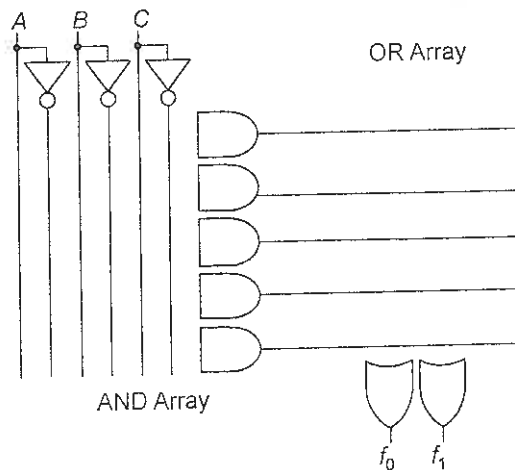Question 10 [5pt]. Implement $f_1(A, B, C) = \sum m(3, 7)$ and $f_2(A, B, C) = \sum m(1, 2, 5)$ using a PLA. Please complete the design with the minimum form.




參考用


注意：背面有試題

※請在答案卷內作答

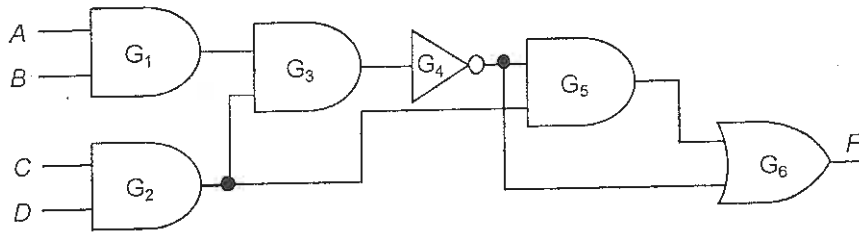
Question 11 [5pt]. Dr. Hunt is debugging a faulty circuit as shown below. According to the specification, with applying the input vector $(A, B, C, D) = (0, 0, 1, 1)$, the output value at F should be 0. However, the actual simulation result is 1. Hunt knows errors come from using wrong gate types. Assume only the following gate types could be misused: $\text{AND} \leftrightarrow \text{NAND}$, $\text{OR} \leftrightarrow \text{NOR}$, $\text{Inverter} \leftrightarrow \text{Buffer}$ (one buffer equals two cascaded inverters), and only one error exists in this circuit. Please indicate all possible erroneous gates. (Please write down the gate instance names.)



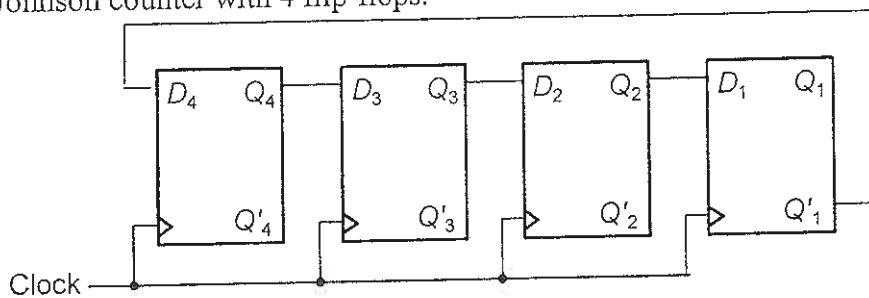Question 12 [5pt]. How many states does a Johnson counter with N flip-flops have? The figure below shows a Johnson counter with 4 flip-flops.



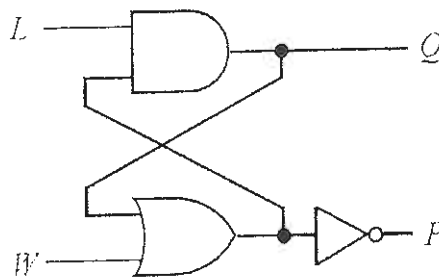
Question 13 [5pt]. A latch design is given below. To guarantee Q will always equal P' , what values cannot be placed on L and W ?




注意：背面有試題

※請在答案卷內作答

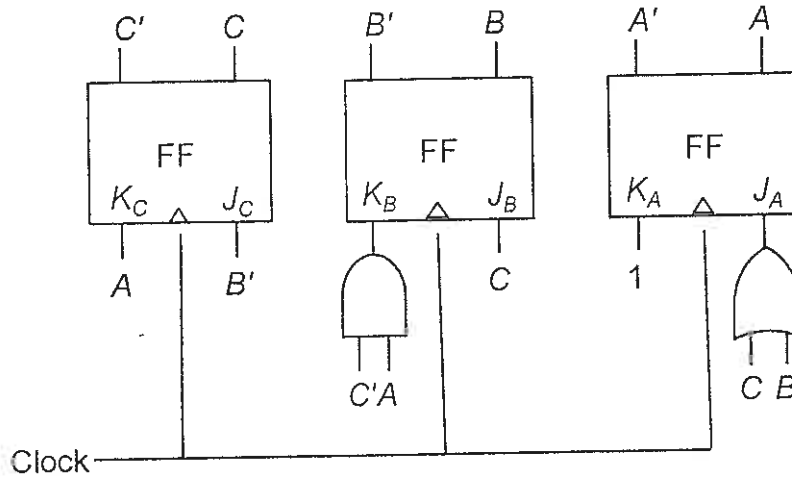Question 14 [5pt]. Professor Pond received the following circuit diagram of a secret counter implemented by J-K flip-flops. Given that the initial state of CBA is 000, please derive the entire counting sequence of this counter. (000 → ??? → ... → 000)



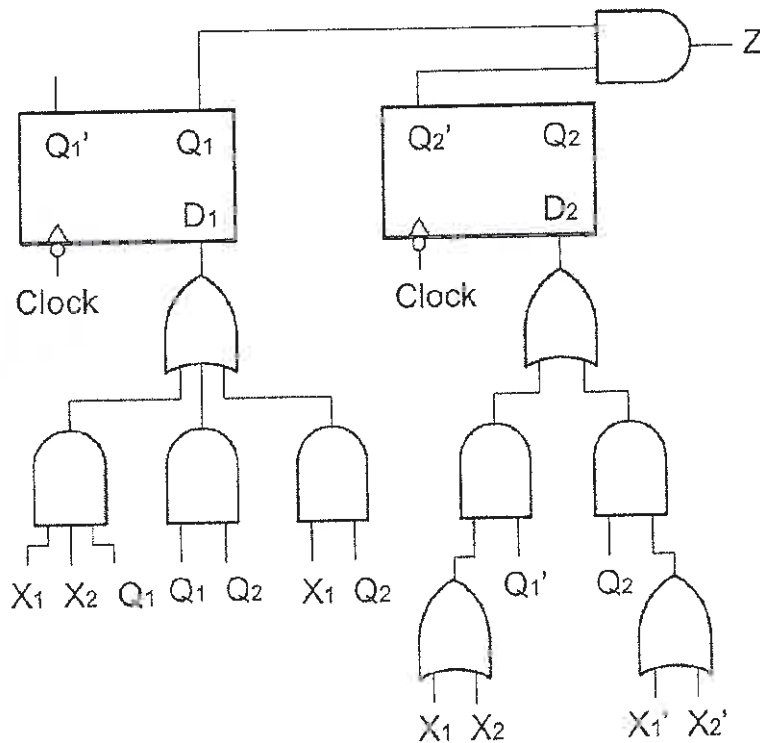Question 15 [5pt]. For a Moore machine as illustrated in the figure below, if $Q_1Q_2=11$, please identify the values of X_1X_2 to make $Z = 1$ in the next state.




參考用

注意：背面有試題


類組：電機類 科目：數位邏輯(300H)

※請在答案卷內作答

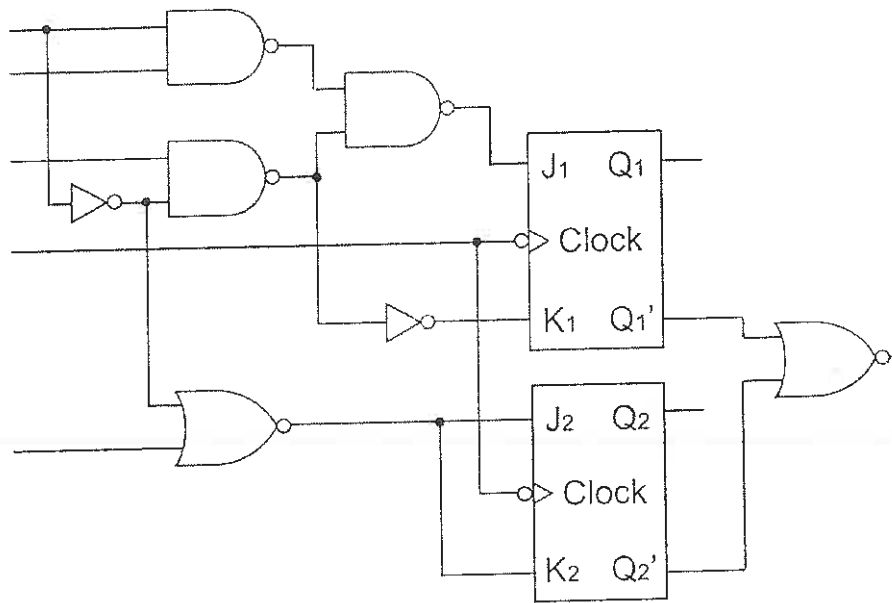Question 16 [5pt]. The figure below shows a Moore machine. The state variables Q_1 and Q_2 can specify four states. Please identify the state (Q_1Q_2) that will loop to itself (a state that is not connected to other states).



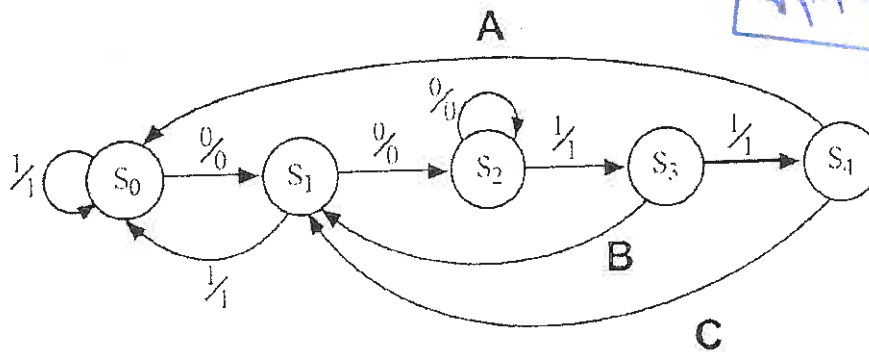Question 17 [5pt]. The state graph of a Mealy sequential circuit is shown in the figure below. The circuit transmits its input, except that it should prevent the sequence 00100 from occurring. Z should be the same as X , except that if the input sequence 00110 occurs, Z should be 1 rather than 0 when the last 0 is received. So the sequence $X=00110$ is replaced with $Z=00111$. Please specify the correct input and output for the three missing transitions (A, B, and C).



參考用

注意：背面有試題

※請在答案卷內作答

Question 18 [5pt]. A Mealy machine has one input X and two outputs (Z_1 and Z_2). The circuit produces an output of $Z_1=1$ whenever the sequence 011 is completed, and an output of $Z_2=1$ whenever the sequence 0111 is completed. The figure below shows the state table. Which state (S_0 to S_3) specifies the state when the machine receives the sequence 011?

State	Next State		$Z_1 Z_2$	
	$X=0$	$X=1$	$X=0$	$X=1$
S_0	S_1	S_0	00	00
S_1	S_1	S_2	00	00
S_2	S_1	S_3	00	10
S_3	S_1	S_0	00	01

Question 19 [5pt]. A Mealy machine has one input and one output that will produce an output of 1 for every second 0 it receives and for every second 1 it receives.

For example:

$$X(\text{input}) = 0 \ 1 \ 1 \ 0 \ 1 \ 1 \ 1 \ 0 \ 0 \ 0 \ 0 \ 1 \ 0 \ 1 \ 1 \ 0 \ 0 \ 1 \ 0 \ 1 \ 1 \ 0 \ 1 \ 0$$

$$Z(\text{output}) = 0 \ 0 \ 1 \ 1 \ 0 \ 1 \ 0 \ 0 \ 1 \ 0 \ 1 \ 1 \ 0 \ 0 \ 1 \ 1 \ 0 \ 0 \ 1 \ 1 \ 0 \ 0 \ 1 \ 1$$

The circuit is implemented using two J-K flip-flops. Which of the following logic expressions can meet the specification of the Mealy machine defined above?

- (a) $J_a=X', K_a=1, J_b=X, K_b=1$
- (b) $J_a=0, K_a=1, J_b=1, K_b=X$
- (c) $J_a=X, K_a=X, J_b=0, K_b=1$
- (d) $J_a=1, K_a=X', J_b=X', K_b=X$
- (e) $J_a=X', K_a=X', J_b=1, K_b=1$
- (f) $J_a=X', K_a=0, J_b=X', K_b=1$

參考

注意：背面有試題

類組：電機類 科目：數位邏輯(300H)

※請在答案卷內作答

Question 20 [5pt].

Which of the following choices contain tables that are equivalent?

(a)

	XY = 00	01	11	10	Z
a	a	c	e	d	0
b	d	e	e	a	0
c	e	a	f	b	1
d	b	c	c	b	0
e	c	d	f	a	1
f	f	b	a	d	1

	XY = 00	01	11	10	Z
a	b	i	c	g	0
b	b	c	f	g	0
c	h	d	d	f	1
d	h	c	e	g	1
e	b	c	i	g	0
f	f	i	i	k	0
g	j	k	g	h	0
h	e	f	c	g	0
i	i	i	i	d	0
j	b	f	c	g	0
k	a	c	e	g	1

(b)

	X = 0	1	
S ₀	S ₃	S ₁	0
S ₁	S ₀	S ₁	0
S ₂	S ₀	S ₂	1
S ₃	S ₀	S ₃	1

	X = 0	1	
A	E	A	1
B	F	B	1
C	E	D	0
D	E	C	0
E	B	D	0
F	B	C	0

(c)

Present State	X = 0		1	
	X = 0	1	X = 0	1
a	h	c	1	0
b	c	d	0	1
c	h	b	0	0
d	f	h	0	0
e	c	f	0	1
f	f	g	0	0
g	g	c	1	0
h	a	c	1	0

Present State	X = 0		X = 1	
	X = 0	X = 1	X = 0	X = 1
a	e	g	0	1
b	d	f	0	1
c	e	c	1	0
d	b	f	0	1
e	g	f	0	1
f	b	d	1	0
g	e	c	1	0

注意：背面有試題

