

1. (20%) Consider the circuit shown in Fig P1.
- (a) (10%) Let $v_s(t) = u(t)$. Find the forced steady-state expression for v_C (∞) in terms of L , R_1 , R_2 , and C .
- (b) (10%) Consider the natural response of the circuit. Let $L=1\text{H}$, $R_1=10\Omega$, $R_2=10\Omega$, and $C=0.1\text{F}$. Would the natural response of the circuit be overdamped, critically-damped, or underdamped? Please explain your answers clearly. (hint: derive the characteristic equation for the differential equation in (2).)

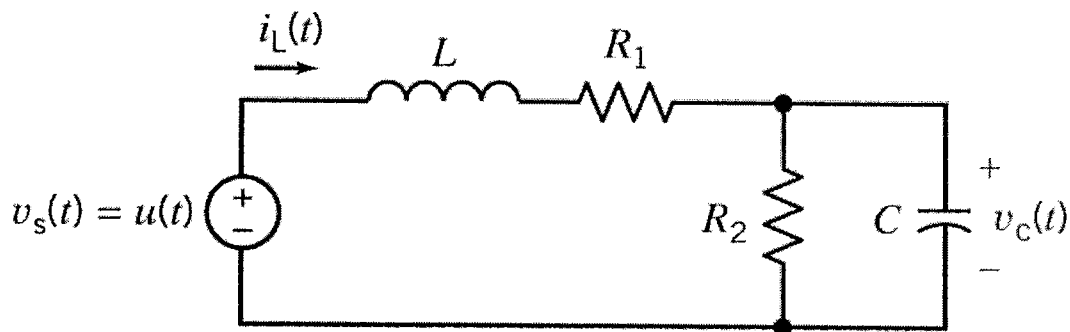


Fig. P1

2. (10%) Consider the Opamp circuit in Fig.P2. Assume the Opamp is ideal. Let $v_s(t) = \cos(\omega t)$. If ω is decreased, the voltage gain $|v_o(t)/v_s(t)|$ will increase or decrease? Please explain your answer clearly. (hint: represent $L=sL$ and $C=1/sC$ to derive the transfer function $|v_o(s)/v_s(s)|$)

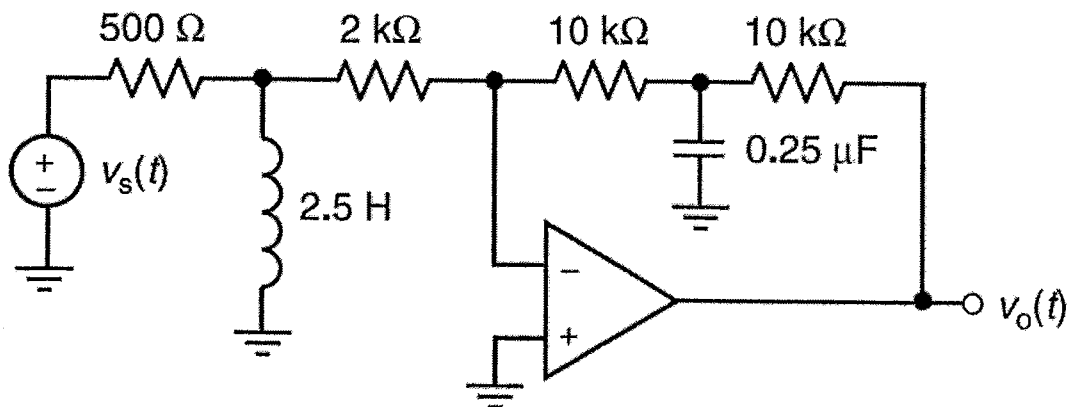


Fig. P2

3. (10%)

- (a) (5%) Set node a as the reference ground. Also, set the node voltage of node b as v_b , the node voltage of node c as v_c , and the node voltage of node d as v_d . Use node method and write a complete set of equations that solve the node voltages v_b , v_c , and v_d .
- (b) (5%) Set node a as the reference ground. For $R_1=1\Omega$, $R_2=2\Omega$, $R_3=3\Omega$, $R_4=4\Omega$, $R_5=8\Omega$, and $I=10\text{mA}$, find all the node voltages and the branch current i as shown in the figure.

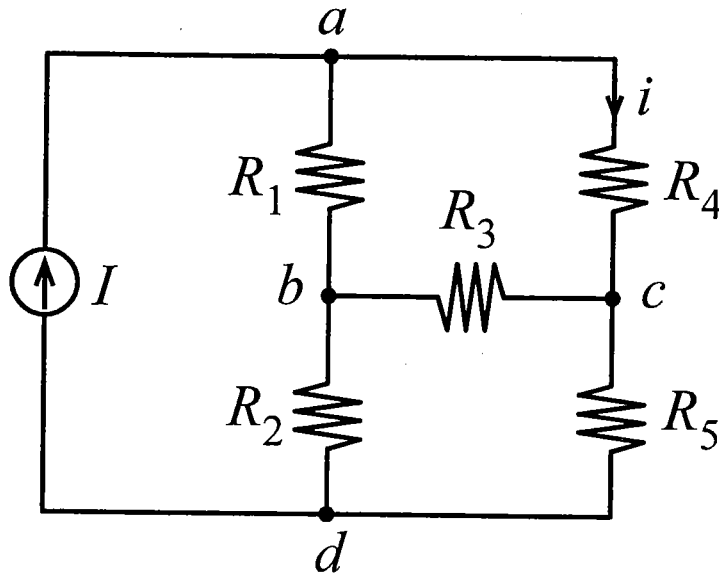


Fig. P3

4. (10%)

(a) (5%) Find the Thevenin equivalent circuit for the following network.

(b) (5%) Write the equation that expresses i as a function of v .

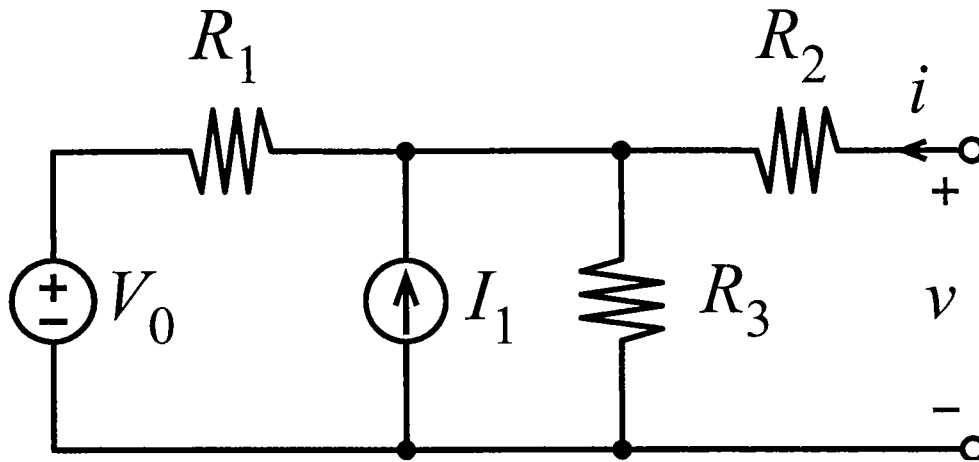


Fig. P4

5. (10%) For the opamp in the following circuit, $v_o = A(v_+ - v_-)$. Find v_{OUT} and i_{OUT} in terms of v_{IN} , A , R_1 , and R_2 .

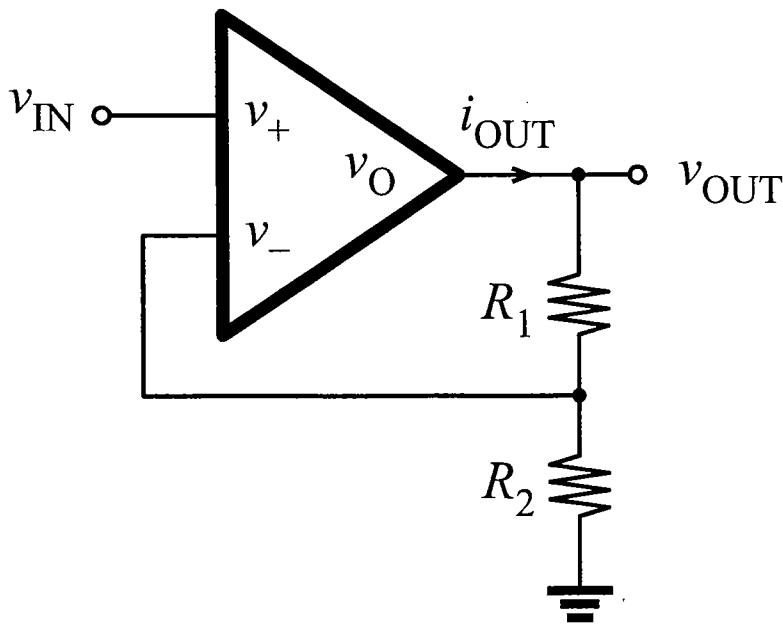


Fig. P5

注意：背面有試題

6.(10%) Use superposition to find the steady-state current $i(t)$ for $R = 10 \text{ Ohm}$, $L = 200 \text{ mH}$, $v_{s1} = 24 \cos(20000t) \text{ V}$, $v_{s2} = 8 \cos(60000t + 30^\circ) \text{ V}$.

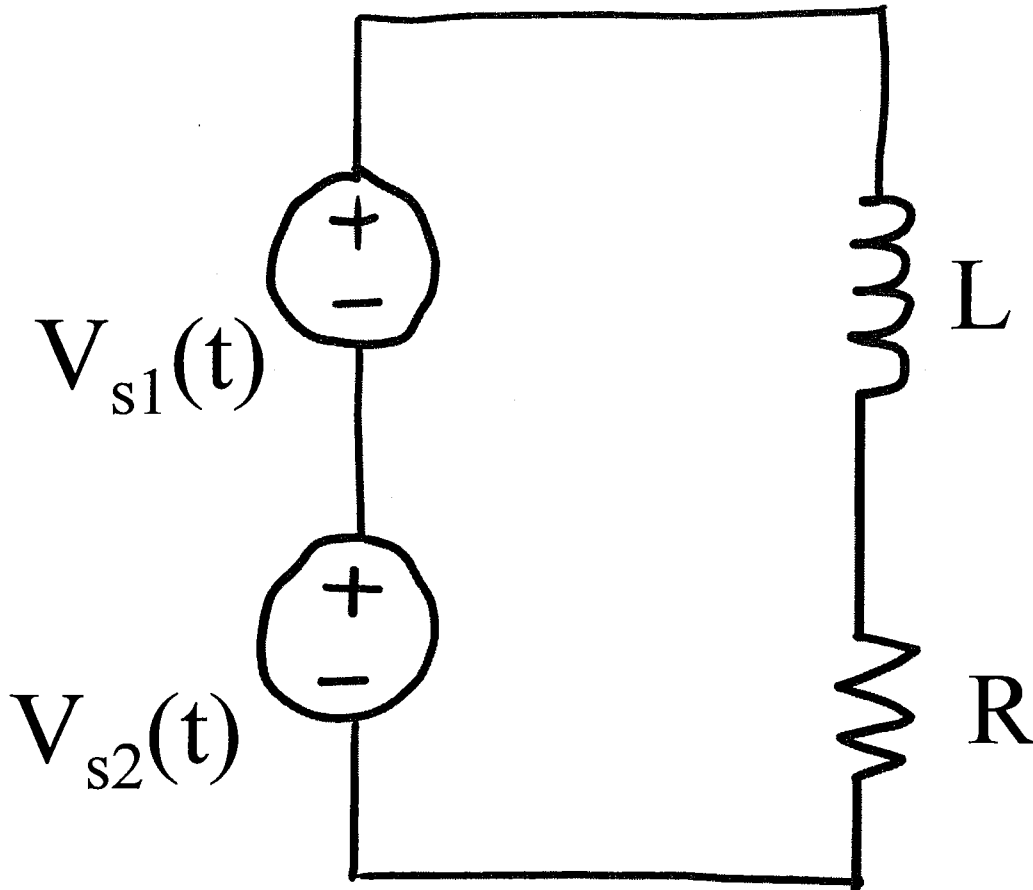


Fig. P6

- 7.(10%) A 240-V rms 60-Hz supply serves a load that is 10 kW (resistive), 15 kVAR (capacitive), and 22 kVAR (inductive). Find:
- the apparent power
 - the current drawn from the supply
 - the kVAR rating and capacitance required to improve the power factor to 0.96 lagging
 - the current drawn from the supply under the new power-factor conditions

8.(10%)

(a) (3%) Draw the circuit topology of an isolated flyback converter.

(b)(7%) This isolated flyback converter operates in the continuous conduction mode with a duty ratio D in PWM control. Use the volt-second balance principle to find the relationship between the input voltage and output voltage.

9.(10%)

(a)(3%) Draw the circuit topology of a buck converter.

(b)(7%) This buck converter operates in PWM control with a duty ratio D . Find the minimum inductance in the boundary condition between the continuous conduction mode and the discontinuous conduction mode.