

1. (5%) (a) Consider the circuit in Figure 1. The ammeter has an internal resistance of 4 Ohms. Find the current i_1 .
 (5%) (b) What is the power dissipated on R_1 ?

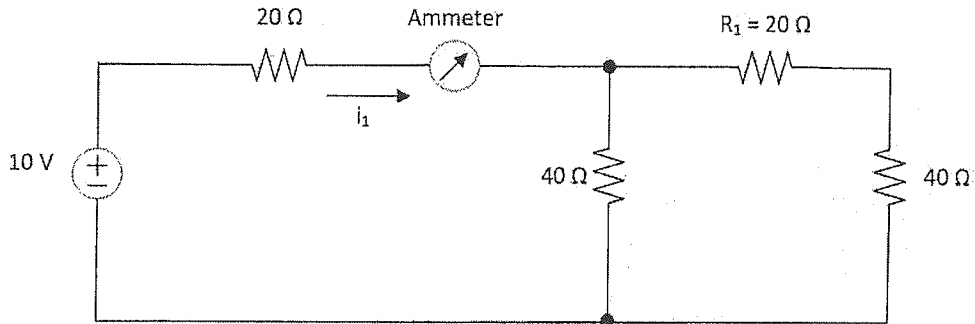


Figure 1.

2. (10%) For the circuit shown in Figure 2, determine the Thévenin and Norton equivalent circuits at terminals a and b.

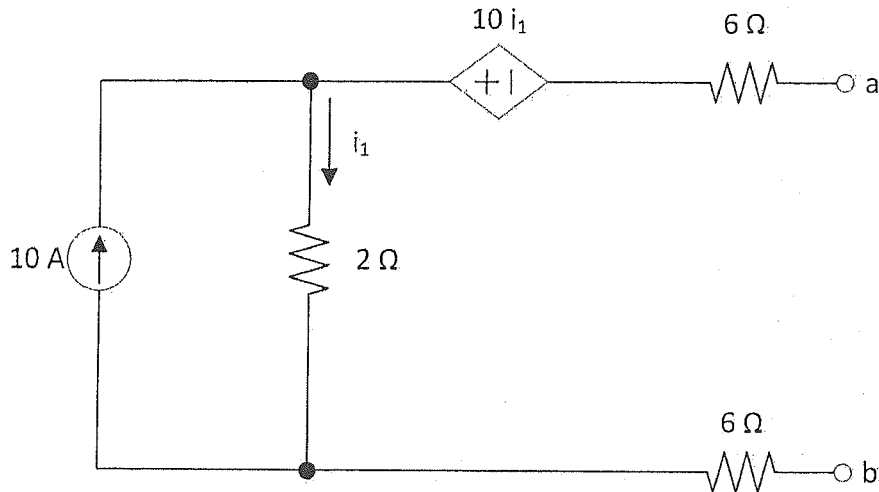


Figure 2.

3. (10%) For the circuit shown in Figure 3, determine $v_c(t)$ for $t > 0$.

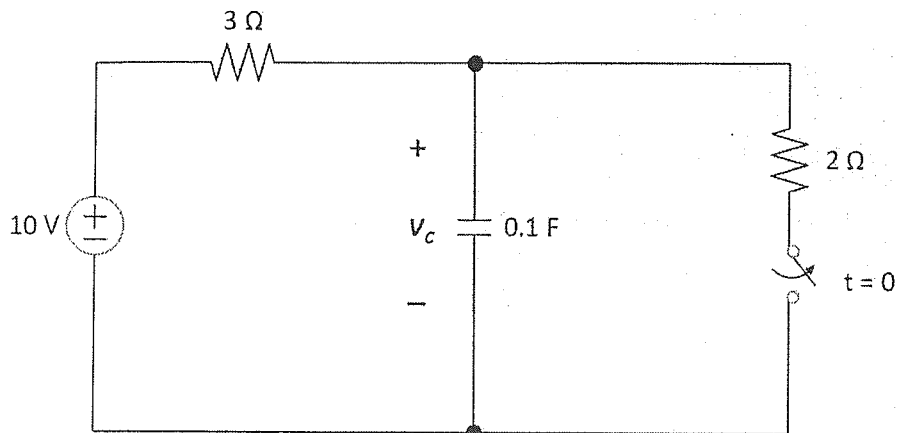


Figure 3.

4. (10%) Figure 4 shows two inductive two-port networks. Fig. 4(a) is a " π " network, and Fig. 4(b) is a "T" network.
- (2%) For the π network, find v_{1P} and v_{2P} as functions of i_{1P} and i_{2P} .
 - (2%) For the T network, find v_{1T} and v_{2T} as functions of i_{1T} and i_{2T} .
 - (6%) How must L_{1P} , L_{2P} , and L_{3P} be related to L_{1T} , L_{2T} , and L_{3T} for both networks to have the same terminal relations?

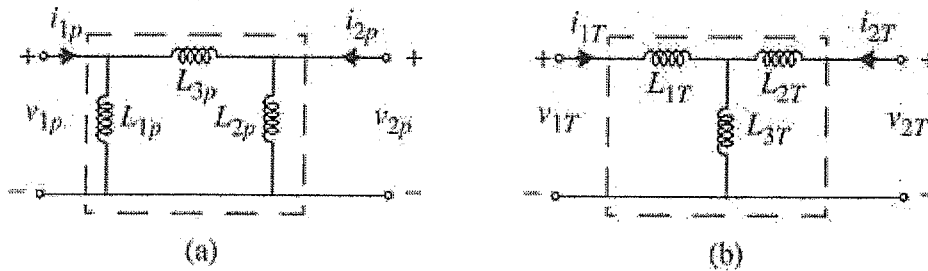


Figure 4.

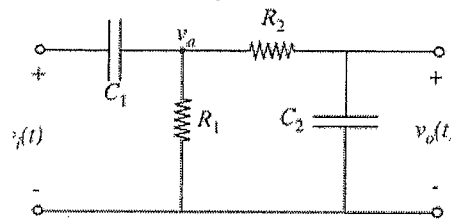


Figure 5.

5. (10%) Consider the second-order circuit containing resistors and capacitors shown in Figure 5. We are interested in deriving $v_o(t)$ for an input of the form $v_i(t) = V_i \cos(\omega t)$. Let $V_o(s)$ and $V_i(s)$ be these Laplace transforms of $v_o(t)$ and $v_i(t)$, respectively, and $R_1 = 1 \text{ k}\Omega$, $R_2 = 1 \text{ k}\Omega$, $C_1 = 1 \text{ mF}$, and $C_2 = 1 \text{ mF}$.
- (4%) Find the transfer function $V_o(s)/V_i(s)$.
 - (6%) Determine the time-domain output voltage $v_o(t)$ if all capacitors are initially uncharged.
6. (20%) A load as shown in Figure 6 has an impedance of $Z=100+j100 \Omega$. Find the parallel impedance Z_p required correct the power factor to (a) 0.95 lagging and (b) 1.0. Assume the generator operates at $\omega = 377 \text{ rad/s}$.


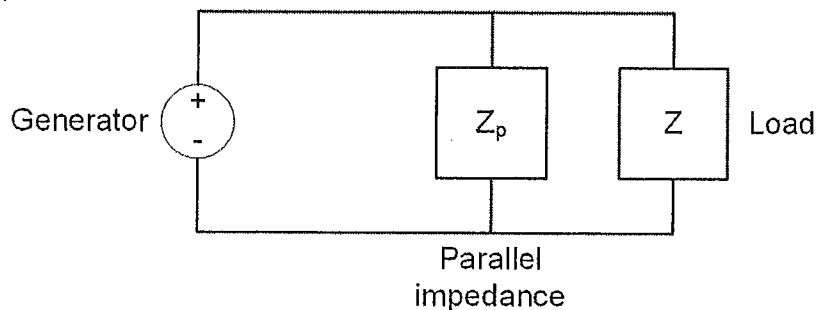


Figure 6.

7. (10%) A balanced three-phase source has a Y-connected source with $v_a = 10 \cos(2t + 30^\circ)$ connected to a three-phase Y load. Each phase of the Y-connected load consists of a $4\text{-}\Omega$ resistor and a 8-H inductor. Each connecting line has a resistance of 2Ω . Determine the total average power delivered to the load.

注意：背面有試題

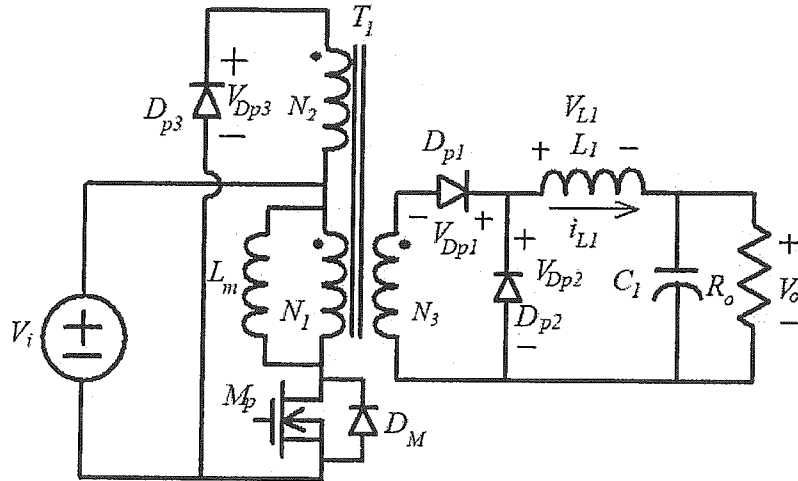8. A forward converter is sketched as follows and operated in continuous conduction mode. Determine:
 (9%) (A) the voltage stresses imposed on diodes D_{P1} , D_{P2} and D_{P3} .
 (3%) (B) the voltage stress imposed on switch M_P .



9. A flyback converter with magnetizing inductance L_m is shown as follows. When it is operated in continuous conduction mode and with a duty ratio of D , determine
 (4%) (A) the v_o/v_i transfer function in terms of D , and
 (4%) (B) the voltage stresses V_{ds} and V_d imposed on switches S_M and D_M , respectively.

