

國立中央大學97學年度碩士班考試入學試題卷

所別：電機工程學系碩士班 電子組、固態組 科目：電子學 共 2 頁 第 1 頁

系統與生醫組、電波組

*請在試卷答案卷(卡)內作答

1. 簡答題 (18分)

Consider the BJT circuits in Fig. 1,

1-1 Please specify the corresponding configuration for each circuit (common-emitter, common-base, or emitter-follower?) (6分)

1-2 Which R_{in} is the largest? Why? Assume that each BJT has the same $\beta_F = 100$, $V_{BE(on)} = V_{EB(on)} = 0.7$ V. (6分)

1-3 Which circuit has a voltage gain always less than unity ($A_v \equiv |v_o/v_{sig}| < 1$)? Why? (6分)

參考用

 


Fig. 1(a)

 


Fig. 1(b)

 


Fig. 1(c)

2. 計算題 (15分)

Consider a common-source MOSFET amplifier in Fig. 2. The transistor has $\mu_n C_{ox}(W/L) = 0.25$ mA/V², $V_t = 1.5$ V, $V_A = 50$ V. Assume the coupling capacitors to be sufficiently large so as to act as short circuits at the signal frequencies of interest.

2-1 Find R_{in} and v_o/v_i . (10分)

2-2 Find the largest allowable input signal to keep the MOSFET in saturation at all times. (5分)

 


Fig. 2

 


Fig. 3

 


Fig. 4

3. 計算題 (15分)

Figure 3 shows a CMOS common-gate amplifier with active-loaded, Q_2 and Q_3 are matched, $\mu_n C_{ox}(W/L) = \mu_p C_{ox}(W/L) = 4$ mA/V², and all transistors have $|V_t| = 0.8$ V, $|V_A| = 16$ V, and the bias current $I = 80$ μ A. Transistor Q_1 has $\chi = 0.25$ for body transconductance g_{mb} . The v_{sig} is a small sinusoidal signal with no dc component.

3-1 Find the values of g_{m1} and g_{mb1} . (5分)

3-2 Find the value of R_{in} . (5分)

3-3 Calculate the voltage gain v_o/v_i . (5分)

4. 計算題 (10分)

Find the values of the voltage gain v_o/v_i and the input resistance R_{in} of the amplifier shown in Fig. 4 assuming $\beta = 100$ and $V_T = 25$ mV. (10分)

洋北工六第

5. 選擇題與計算題 (12分)

Figure 5 shows a feedback amplifier which design parameters are listed as follows, $g_{m1} = g_{m2} = 5 \text{ mA/V}$, $R_D = R_S = 10 \text{ k}\Omega$, and $R_F = 90 \text{ k}\Omega$. Neglect r_o and body effect.

5-1 Identify the feedback topology to be used. (A) Shunt-Series, (B) Series-Series, (C) Shunt-Shunt, (D) Series-Shunt. (3分)

5-2 Find the overall gain I_o/I_s . (9分)

 


Fig. 5

參考用

6. 作圖題 (5分)

Sketch a CMOS implementation of a clocked SR flip-flop. The clock signal is denoted by ϕ .

7. 問答題 (5分)

As shown in Fig. 6, the Content Addressable Memory (CAM) cell is implemented by an SRAM cell with the Tag-Compare Portion. During the precharge phase, the match line (ML) is charged to V_{DD} . Find the final comparison result of the ML when the logic value of $(n1, DL) = (1, 1)$.

8. 問答題 (10分)

As shown in Fig. 7, which type of logic gate does the circuit implement? Sketch the output waveform of the node Q2.

 


Fig. 6

 


Fig. 7

9. 計算題 (10分)

A CMOS Inverter with an additional 0.1 pF capacitance load, the design parameters of this CMOS Inverter are listed as following: $(W/L)_n = 10$, $(W/L)_p = 20$, $\mu_n C_{ox} = 2\mu_p C_{ox} = 0.2 \text{ mA/V}^2$, $V_m = |V_{\phi}| = 1 \text{ V}$, $V_{DD} = 5 \text{ V}$. Assume the gate-drain overlap capacitance and the drain-body capacitance are zero.

9-1 Find the propagation delay t_{PHL} . (5分)

9-2 Find the dynamic power dissipation when clocked at 50 MHz . (5分)

注意：背面有試題