

1. Assume the transistor in the circuit in Fig.1 has parameters of  $V_{BE(on)} = 0.7$  V, current gain  $\beta = 120$ , thermal voltage  $V_T = 0.026$  V, and Early voltage  $V_A = 100$  V. The resistors are set as  $R_1 = 1$  K $\Omega$  and  $R_2 = 1$  K $\Omega$ .
  - (a) Determine the Q-point (working point) of transistor ( $V_{CEQ}$ ,  $I_{CQ}$ ). (5%)
  - (b) Define the load line equation, sketch the load line and plot the Q-point for transistor. (5%)
  - (c) Determine the mid-band small-signal trans-resistance  $R_{in} = v_o/i_s$ . (5%)

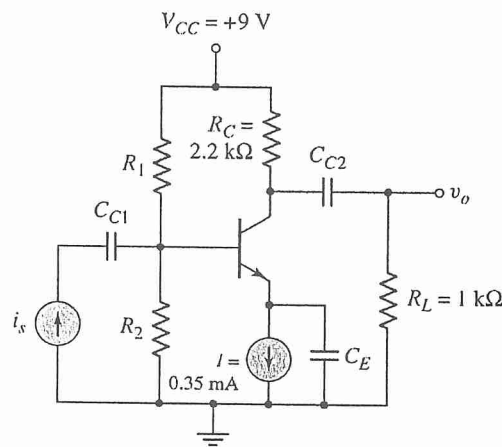


Fig. 1

2. A current-to-voltage converter with a phototransistor that converts light intensity into an output current  $i_C$  is shown in Fig. 2(a). The transistor has a finite capacitor  $C_{CE}$  and must be biased as shown in Fig. 2(a). The current-to-voltage converter realized using an op-amp has a finite open-loop differential gain  $A_{od}$ . The transistor output versus input characteristics are shown in Fig. 2(b).
  - (a) Determine the input resistance  $R_{in}$  of current-to-voltage converter. (5%)
  - (b) Define the load line equation and sketch the load line for transistor. (5%)
  - (c) Determine the small-signal trans-impedance  $Z_{in} = v_o/i_C$  of current-to-voltage converter under considering the frequency response. (10%)
  - (d) Determine the higher corner (-3 dB) frequency  $f_H$  of  $Z_{in}$ . (5%)

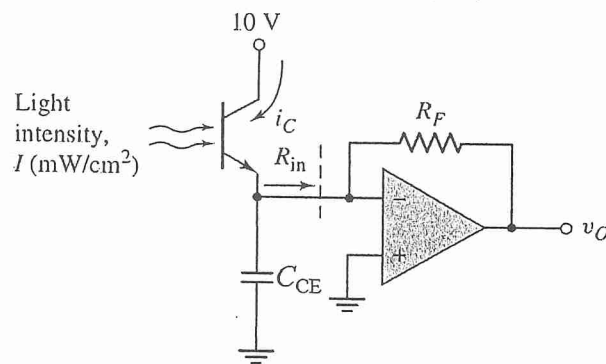


Fig. 2(a)

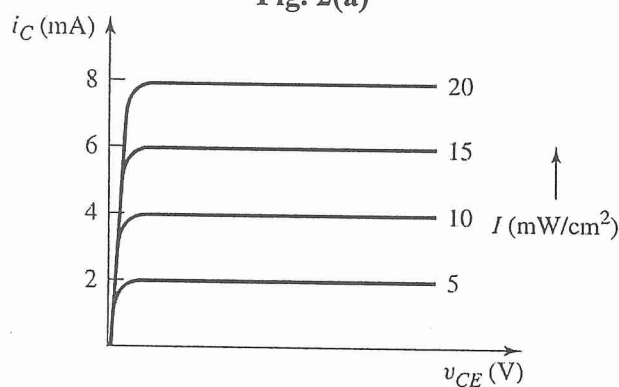


Fig. 2(b)

參考用

注意：背面有試題

參考用

3. The circuit in Fig. 3(a) is used to drive an LED with a voltage source. Assume the op-amp is ideal. The resistors are set as  $R_1 = 1 \text{ K}\Omega$ ,  $R_F = 1 \text{ K}\Omega$ , and  $R_2 = 1 \text{ K}\Omega$ . The LED has piecewise linear parameter of turn on (cut-in) voltage  $V_r = 3 \text{ V}$  and forward diode resistance  $r_f = 0 \Omega$ . If the triangular wave, shown in Fig. 3(b), is applied.
- (a) Plot  $i_D$  versus  $v_I$  for the circuit. (5%)  
(b) Plot  $v_O$  versus time for the circuit. (5%)

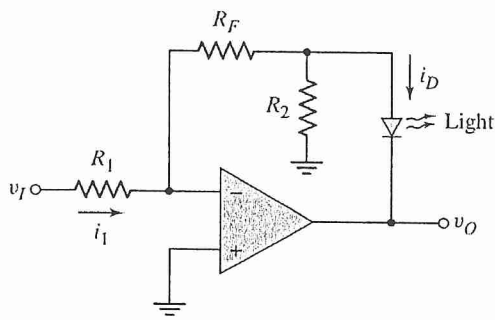


Fig. 3(a)

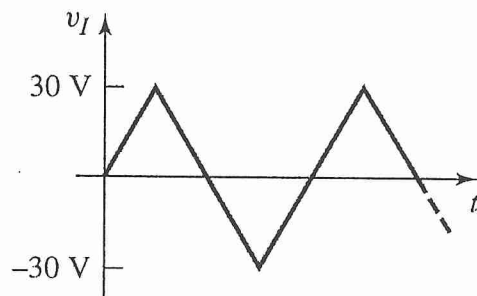


Fig. 3(b)

4. Consider the circuit shown in Fig. 4 where  $R = 19 \text{ k}\Omega$ .  $V$  is  $10 \text{ V}$  which is superimposed a  $60 \text{ Hz}$  sinusoid of  $1\text{-V}$  peak amplitude. The diode has a  $0.5\text{-V}$  voltage drop at  $0.5\text{-mA}$  current. The constant  $n$  in diode equation is 2 for silicon. Calculate the amplitude of the sine-wave across the diode. (15%)



Fig. 4

5. An enhancement-type NMOS transistor with threshold voltage  $V_t = 2 \text{ V}$  has its source terminal grounded and a  $3\text{-V}$  dc source connected to the gate. The drain is connected to a dc voltage of  $3 \text{ V}$ . The process trans-conductance parameter,  $\mu_n C_{ox}$ , is  $40 \mu\text{A}/\text{V}^2$ . The width and the length of the channel region are  $W = 100 \mu\text{m}$  and  $L = 2 \mu\text{m}$ , respectively. Neglect the dependence of  $i_D$  on  $V_{GS}$  in saturation. Find the drain current. (20%)
6. Calculate the unity-gain frequency  $f_T$  for the n-channel MOSFET whose the capacitance between gate-source and gate-drain,  $C_{gs}$  and  $C_{gd}$ , are  $30 \text{ fF}$  and  $2 \text{ fF}$ , respectively. Assume that the trans-conductance  $g_m$  is  $0.2 \text{ mA}/\text{V}$ . (15%)

注意：背面有試題