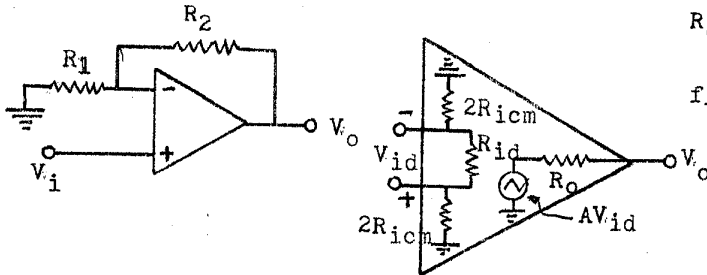


系所別: 光電科學研究所 科目: 電子學

1. Consider an op-amp having $f_t = 1 \text{ MHz}$, $R_{id} = 1 \text{ M}\Omega$, and $R_{icm} = 100 \text{ M}\Omega$. Find the input impedance of a noninverting amplifier with a nominal gain of 100. Assuming that




$R_o = 0, R_1 \ll R_{icm}, \frac{R_2}{R_{id}} \ll A.$


f_t : unity-gain bandwidth.

(20%)

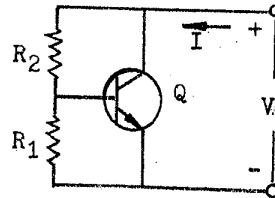2. In the circuit as shown. Find the values of V and the incremental resistance for $R_1 = R_2 = 1 \text{ k}\Omega$. $I = 10 \text{ mA}$, $\beta = 100$, and $V_{BE} = 0.7 \text{ V}$.




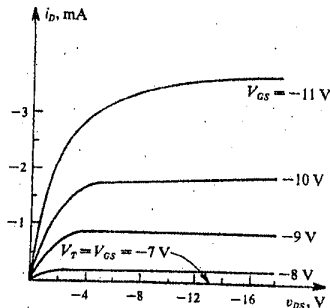3. Employing the MOSFET characteristic curves of Figure, show how saturated drain current values I_{DSS} can be obtained and from them other I_{DS} drain current values in saturation. (20%)



參考用

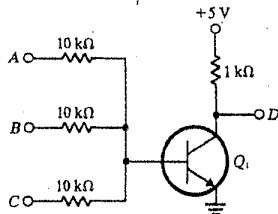4. Prove that the circuit of the Figure is a NOR gate. Ignore the V_{BE} drop, leakage currents, and V_{CES} and assume $\beta \geq 50$, 0V and 5V logic levels, and no external loading. (20%)



5. Design a collector-coupled flip-flop using transistors with $\beta \geq 20$. Assume $V_{CC} = +10 \text{ V}$ and obtain a minimum high-level output voltage of 9V. Ignore V_{BES} and V_{CES} drops. (20%)

