
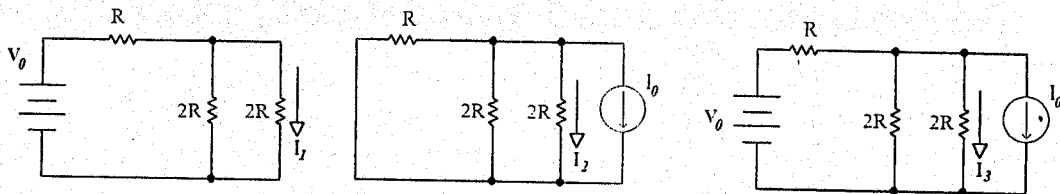


所別：光電科學研究所碩士班 一般生 科目：電子學  
學位在職生

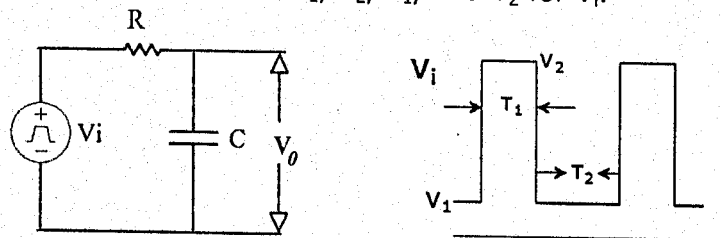
15% 1. Find the currents,  $I_1$ ,  $I_2$ , and  $I_3$  in terms of  $V_0$ ,  $I_0$ , and  $R$ . Then, express the relation among  $I_1$ ,  $I_2$ , and  $I_3$ .




15% 2. Refer to the circuit below. Please discuss the characteristics of the output  $V_0$  in terms of the parameters of  $V_1$ ,  $V_2$ ,  $T_1$ , and  $T_2$  for  $V_1$ .



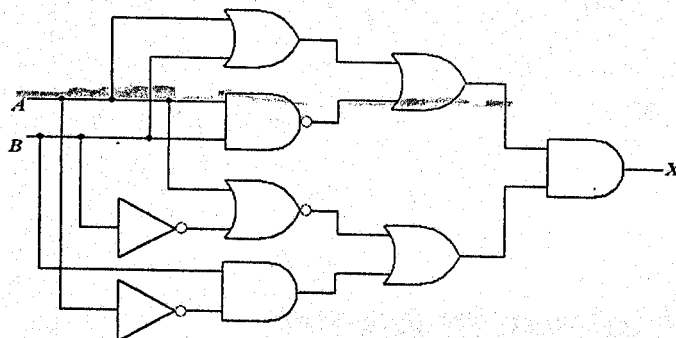15% 3. Simplify the logic circuit with as few logic gates as possible (AND, OR, and NOT gates only).  $A$  and  $B$  are two input ports, and  $X$  is the output port.



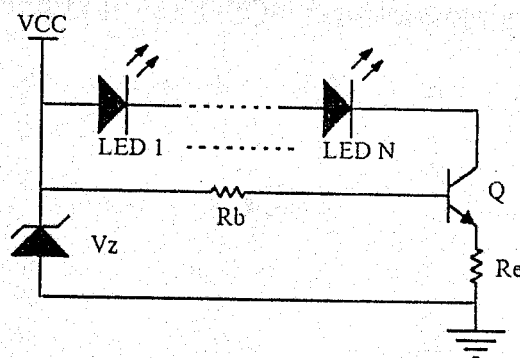20% 4. Derive the electric current,  $I_f$  through LEDs. If each LED has a voltage drop  $V_f$ , evaluate the maximum possible number of LEDs.




注意：背面有試題

所別：光電科學研究所碩士班 一般生 科目：電子學  
學位在職生

20% 5. Please design the BJT circuit, and find out  $R_1, R_2, R_B, R_C, R_E$  :

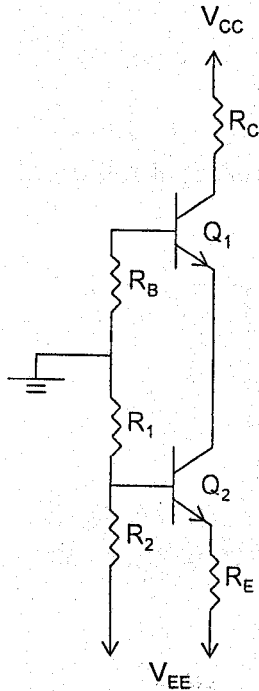- (1) When current gain  $\beta$  is infinity,  $I_{C1} = 0.1\text{mA}$ ,  $V_{RE} = 2\text{V}$  and  $V_{CE1} = 1.5\text{V}$  ;  
 (2) When current gain  $\beta$  is 50,  $V_{CE1} = 2.5\text{V}$  and  $V_{RE}$  reduced 5%



15% 6. Please find out these circuit symbols :

- (1) Zener Diode (2) npn BJT (3) p-channel MOSFET  
 (4) n-channel depletion-type MOSFET (5) n-channel JFET

