

- 一. (20%) 計算題 The per-phase equivalent circuit of a non-salient synchronous generator is as shown in Fig. 1. The generator is connected to the infinity bus with $\tilde{V}_t = 120\angle 0^\circ$ (V) and $\tilde{E}_f = E_f\angle\delta = 207\angle 25^\circ$ (V):
- (一) Find \tilde{I}_a , power factor, P and Q . (10%)
- (二) If the real power P is fixed, and E_f is increased from 207 V to 227 V, find the new power angle δ and reactive power Q . (10%)

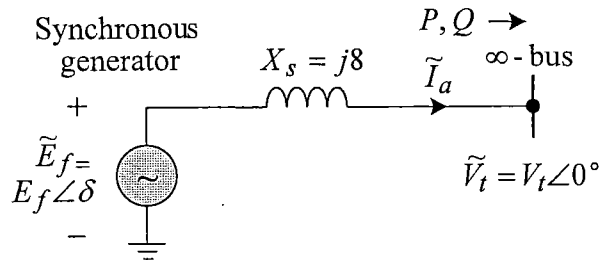


Fig. 1

- 二. (10%) 申論題 Consider a transformer and an induction motor.
- (一) Draw the equivalent circuits of a transformer and an induction motor. (5%)
- (二) Describe their differences and similarities. (5%)
- 三. (30%) 計算題 A salient-pole generator without dampers is rated 20 MVA, 13.8 kV and has a direct-axis sub-transient reactance of 0.25 per unit. The negative- and zero-sequence reactances are, respectively, 0.35 and 0.10 per unit. The neutral of the generator is solidly grounded. With the generator operating unloaded at rated voltage with $E_{an} = 1.0\angle 0^\circ$ per unit, a single line-to-ground fault occurs at the machine terminal, which then have per-unit voltages to ground, $V_a = 0$ $V_b = 1.013\angle -102.25^\circ$ $V_c = 1.013\angle 102.25^\circ$. Determine the sub-transient current in the generator and the line-to-line voltages for sub-transient conditions due to the fault.
- 四. (15%) 申論題 Consider the power flow study of a transmission system.
- (一) Let one bus without any loads and any generators. Is this bus be classified as a load bus or a generator bus? Please provide your justifications. (5%)
- (二) Let all transmission lines be pure inductive. Will any active power loss exist in this transmission system? (5%)
- (三) Please state these conditions such that the conventional power flow can be solved by the decoupled method and the fast-decoupled method. (5%)
- 五. (10%) 計算題 Find the following optimal economic dispatch problem by neglecting system losses and generator limit if the total demand is 800 MW. Cost functions of these three generator in \$/MW Hr are $C_1(P_1) = 500 + 5.3P_1 + 0.004P_1^2$; $C_2(P_2) = 400 + 5.5P_2 + 0.006P_2^2$; and $C_3(P_3) = 200 + 5.8P_3 + 0.009P_3^2$.
- 六. (15%) 申論題 Consider the transient stability of the one-machine-infinite-bus system. Please justify your answer which of these following methods can improve the transient stability. (i) Increase of system voltages, and use of automatic voltage regulators; (ii) Use of quick response excitation systems; (iii) Compensation for transfer reactance; (iv) Use of high-speed circuit breakers which reduce the fault duration time; (v) Increase the system inertia.